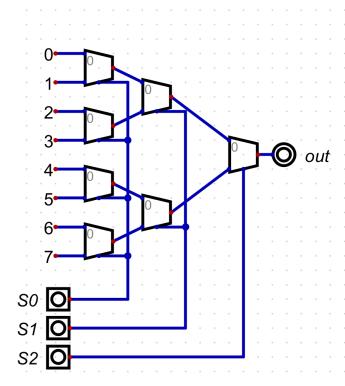





## Q2-)



0 0 0 0 0 0 0 0 1 0 0 1 0 1 0 0 1 0 1 1 0 0 1 1 0 0 1 1 1 0 0 1 1 1 0 0 1 1 1 1 1 0 1 1 1 1 1 1	S2	S1	S0	out2	out1	out0				
0 1 0 0 1 0   0 1 1 0 1 1   1 0 0 1 0 0   1 0 0 1 0 0 1   1 1 0 1 1 0 1 1 0	0	0	0	0	0	0				
0 1 1 0 1 1   1 0 0 1 0 0   1 0 1 1 0 1   1 1 0 1 1 0 1	0	0	1	0	0	1				
1 0 0 1 0 0   1 0 1 1 0 1   1 1 0 1 1 0	0	1	0	0	1	0				
1 0 1 1 0 1 1 1 0 1 1 0	0	1	1	0	1	1				
1 1 0 1 1 0	1	0	0	1	0	0				
	1	0	1	1	0	1				
1 1 1 1 1 1	1	1	0	1	1	0				
	1	1	1	1	1	1				

All possible solution	ons					×
out <sub>2</sub> = S2						
out <sub>1</sub> = S1						
out <sub>o</sub> = S0						



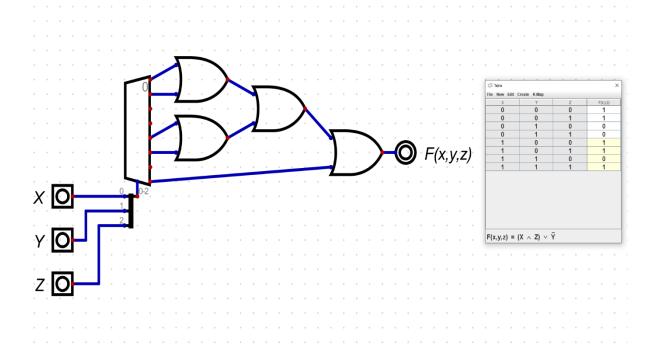

## Q4-)

